
Projeto de Sistemas Digitais

- Arthur Alexandre Nascimento
- Eduardo Vinicius Betim
- Fábio Pereira dos Santos
- Rafael Francisco Réus


Algoritmo de divisão

```
Algoritmo divseq
  1 Início{
       A \leftarrow \text{ent1}; B \leftarrow \text{ent2}; \text{cont} \leftarrow 0; \text{pronto} \leftarrow 0;
       if B!=0 then {
         while A >= B \{
            cont \leftarrow cont + 1;
        A \leftarrow A - B;
         quoc \leftarrow cont; resto \leftarrow A;
 8
         pronto\leftarrow 1; erro\leftarrow 0;
 9
10
       else
11
         pronto\leftarrow1; erro\leftarrow1;
12 }
```


FSMD

 


Bloco Operativo

 


State Machine Viewer

 


RTL Viewer - Topo

 

RTL Viewer - BO

 

RTL Viewer - BC

 

Comparação N = 4 e N = 8

Flow Status	Successful - Wed Nov 25 16:51:03 2020
Quartus II 64-Bit Version	13.0.1 Build 232 06/12/2013 SP 1 SJ Web Edition
Revision Name	divisor
Top-level Entity Name	divisor
Family	Cyclone II
Device	EP2C35F672C6
Timing Models	Final
Total logic elements	33 / 33,216 (< 1 %)
Total combinational functions	21 / 33,216 (< 1 %)
Dedicated logic registers	26 / 33,216 (< 1 %)
Total registers	26
Total pins	21 / 475 (4 %)
Total virtual pins	0
Total memory bits	0 / 483,840 (0 %)
Embedded Multiplier 9-bit elements	0 / 70 (0 %)
Total PLLs	0/4(0%)


Flow Status	Successful - Wed Nov 25 16:55:59 2020
Quartus II 64-Bit Version	13.0.1 Build 232 06/12/2013 SP 1 SJ Web Edition
Revision Name	divisor
Top-level Entity Name	divisor
Family	Cyclone II
Device	EP2C35F672C6
Timing Models	Final
Total logic elements	50 / 33,216 (< 1 %)
Total combinational functions	34 / 33,216 (< 1 %)
Dedicated logic registers	46 / 33,216 (< 1 %)
Total registers	46
Total pins	37 / 475 (8 %)
Total virtual pins	0
Total memory bits	0 / 483,840 (0 %)
Embedded Multiplier 9-bit elements	0 / 70 (0 %)
Total PLLs	0/4(0%)

Comparação N = 4 e N = 8


	Data Port	Clock Port	Rise	Fall	Clock Edge	Clock Reference
1	erro	clk	6.750	6.750	Rise	clk
2	pronto	dk	7.227	7.227	Rise	dk
3	∨ quoc[*]	clk	6.392	6.392	Rise	dk
1	quoc[0]	dk	6.392	6.392	Rise	dk
2	quoc[1]	clk	6.585	6.585	Rise	dk
3	quoc[2]	dk	6.603	6.603	Rise	dk
4	quoc[3]	clk	6.600	6.600	Rise	dk
4	✓ resto[*]	clk	6.342	6.342	Rise	dk
1	resto[0]	clk	6.402	6.402	Rise	dk
2	resto[1]	dk	6.342	6.342	Rise	dk
3	resto[2]	dk	6.595	6.595	Rise	dk
4	resto[3]	dk	6.610	6.610	Rise	clk

	Data Port	Clock Port	Rise	Fall	Clock Edge	Clock Reference
1	erro	clk	6.613	6.613	Rise	clk
2	pronto	clk	7.186	7.186	Rise	dk
3	✓ quoc[*]	clk	6.270	6.270	Rise	dk
1	quoc[0]	clk	6.370	6.370	Rise	dk
2	quoc[1]	clk	6.358	6.358	Rise	dk
3	quoc[2]	clk	6.270	6.270	Rise	dk
4	quoc[3]	clk	6.411	6.411	Rise	dk
5	quoc[4]	clk	6.523	6.523	Rise	dk
6	quoc[5]	clk	6.528	6.528	Rise	dk
7	quoc[6]	clk	6.357	6.357	Rise	dk
8	quoc[7]	clk	6.396	6.396	Rise	dk
4	✓ resto[*]	clk	6.333	6.333	Rise	dk
1	resto[0]	clk	6.370	6.370	Rise	dk
2	resto[1]	clk	6.333	6.333	Rise	clk
3	resto[2]	clk	6.838	6.838	Rise	clk
4	resto[3]	clk	6.351	6.351	Rise	clk
5	resto[4]	clk	6.582	6.582	Rise	dk
6	resto[5]	clk	6.550	6.550	Rise	dk
7	resto[6]	clk	6.840	6.840	Rise	clk
8	resto[7]	clk	6.370	6.370	Rise	clk


Simulação 12 / 3 - 4 bits

 

Simulação 12 / 5 - 4 bits

 

Simulação 12 / 3 - 8 Bits

 

Conclusão

 Aumento de aprox. 50% na quantidade de elementos lógicos comparando 4 e 8 bits.

O tempo mínimo de clock até a saída diminui levemente na versão com 8 bits.

Fim